

Verification of Combinational and Sequential Circuits in LEAN3

Zahir Bingen | Informatica



Universiteit
Leiden
The Netherlands

Index

1. Introduction

2. Methodology

3. Demo

- Logic Gates
- Multiplexer
- Full-Adder
- Shifter
- Memory
- Counter
- Case Study: Sequence Recognizer

4. Conclusion

5. Challenges and Future Work

Introduction

- Motivation
- Simulation vs Formal Verification
- LEAN3
- Specifications and Implementations
- Combinational and Sequential Circuits
 - Logic Gates (Combinational)
 - Multiplexer (Combinational)
 - ...
 - Flip Flops (Sequential)
 - ...

Methodology

1. Specification creation
2. Specification functionality proof
 - Choose the orientation of input/output
 - Check for existence of output
 - Check whether the output is precisely defined (unique)
3. Implementation of specification
4. Compliance proof
 - Check whether the implementation complies with the specification

Logic Gates

a_1	a_2	o
0	0	0
0	1	0
1	0	0
1	1	1

Table 4: Truth table of a 2-input AND-gate

a_1	a_2	o
0	0	0
0	1	1
1	0	1
1	1	1

Table 3: Truth table of a 2-input OR-gate


a	o
0	1
1	0

Table 2: Truth table of a NOT-gate


a_1	a_2	a_3	o
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

Table 4: Truth table of a 3-input XOR-gate

2_1 Multiplexer 1-bit

 

2_1 Multiplexer n-bit

 


Full-Adder 1-bit

A	B	CIN	SUM	COUT
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1


$$\text{SUM} = (A + B + \text{CIN}) \% 2$$
 
$$\text{COUT} = ((A + B + \text{CIN}) >= 2)$$



Full-Adder n-bit
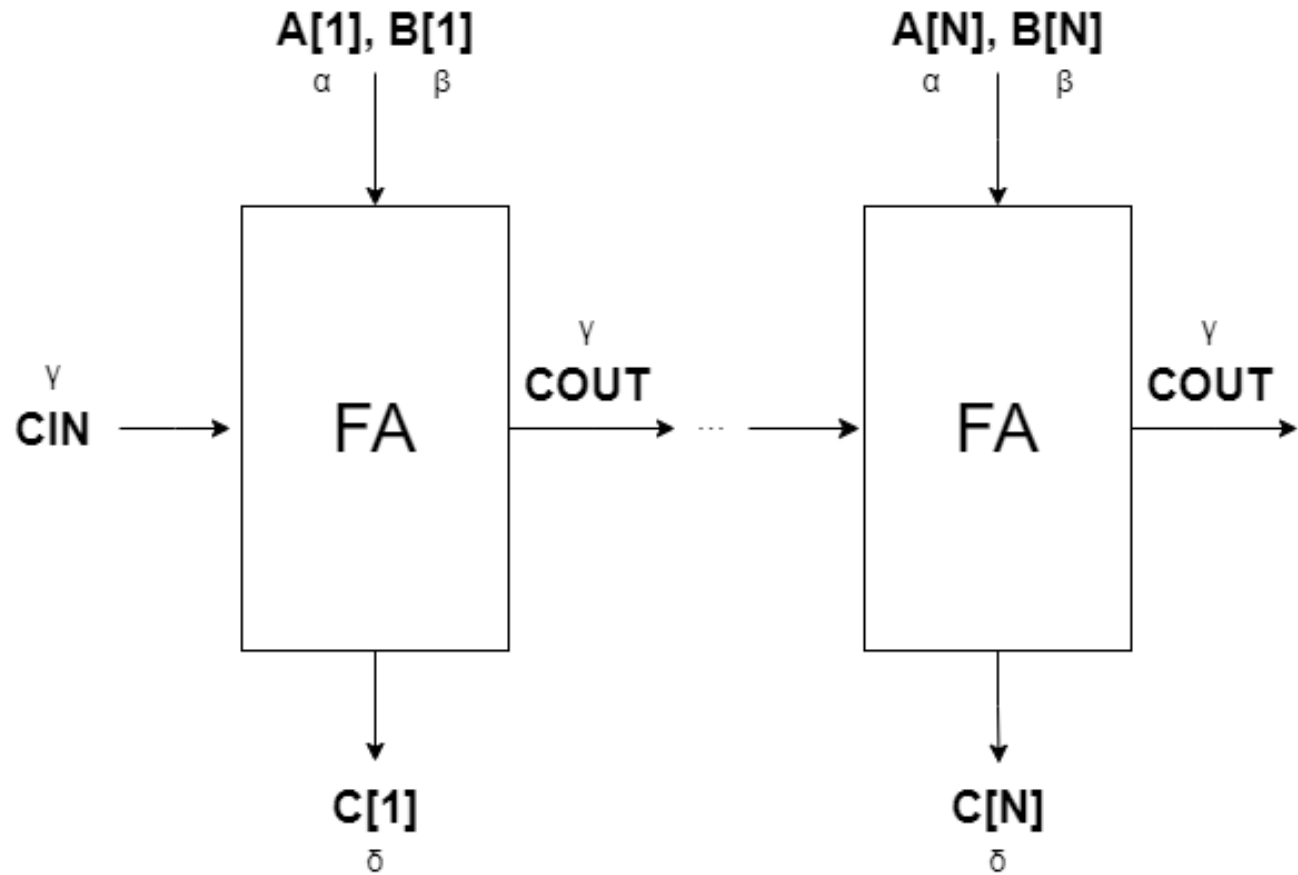
$$\text{SUM} = (A + B + \text{CIN}) \% 2^n$$
$$\text{COUT} = ((A + B + \text{CIN}) \geq 2^n)$$




Shifter

- Right shift: shift all bits to the right, left-most bit is 0
- Left shift: shift all bits to the left, right-most bit is 0

```
def lsh_spec {n : ℕ} (A OUT : array n bool) : Prop :=  
  OUT = ⟨λ i, if h : i.val + 1 < n then A.read ⟨i.val + 1, h⟩ else ff⟩  
def rsh_spec {n : ℕ} (A OUT : array n bool) : Prop :=  
  OUT = ⟨λ i, if h : i.val > 0 ∧ i.val - 1 < n then A.read ⟨i.val - 1, h.right⟩  
    else ff⟩
```

Shifter

IF D then RSH else LSH

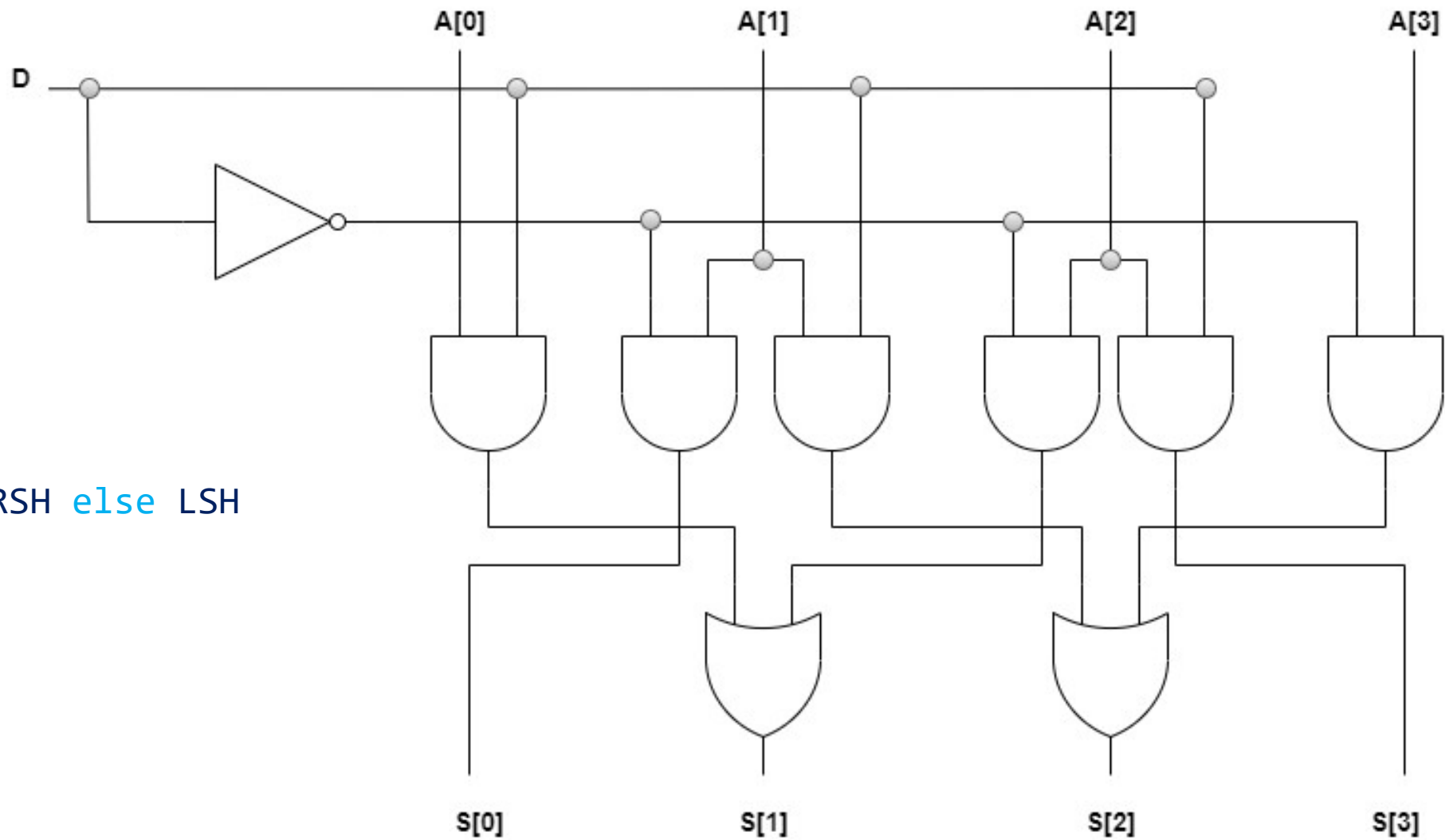

Memory

- Signals (functions of $\mathbb{N} \rightarrow \alpha$)
- Underspecified (initial value?)
- Uniqueness of output?

```
def stream ( $\alpha$  : Type) :=  $\mathbb{N} \rightarrow \alpha$ 
```

```
def signal :=  $\mathbb{N} \rightarrow \text{bool}$ 
```

```
def sig_n (n :  $\mathbb{N}$ ) :=  $\mathbb{N} \rightarrow \text{array } n \text{ bool}$ 
```

T	D	S	M	O
T	*	0	0	0
T+1			0	
...				
...	d	1	*	*
...			d	d
...				

$\forall t : \mathbb{N},$

$(S\ t = \text{tt} \rightarrow M\ (t+1) = D\ t) \wedge$

$(S\ t = \text{ff} \rightarrow M\ (t+1) = M\ t)$

Program Counter

- Memory component attached with an adder
- Hard to implement in LEAN3
- Create a single component like the memory implementation
- If reset signal is true at time t , then at $t+1$ counter is reset
- If reset signal is false at time t , then at $t+1$ counter is incremented by 1

Case Study: Sequence Recognizer

- Verification of Binary Sequence Detector design by Alberto I. Leibovich and Pablo E. Leibovich
- Recognizes the sequence binary sequence “101”
- Changes to state diagram

Actual State	Next State		Output
	X = 0	X = 1	
S ₀	S ₀	S ₁	0
S ₁	S ₂	S ₁	0
S ₂	S ₀	S ₃	0
S ₃	S ₀	S ₃	1

Table 1. Transition Table


 


Figure 1. State Diagram

Case Study: Sequence Recognizer

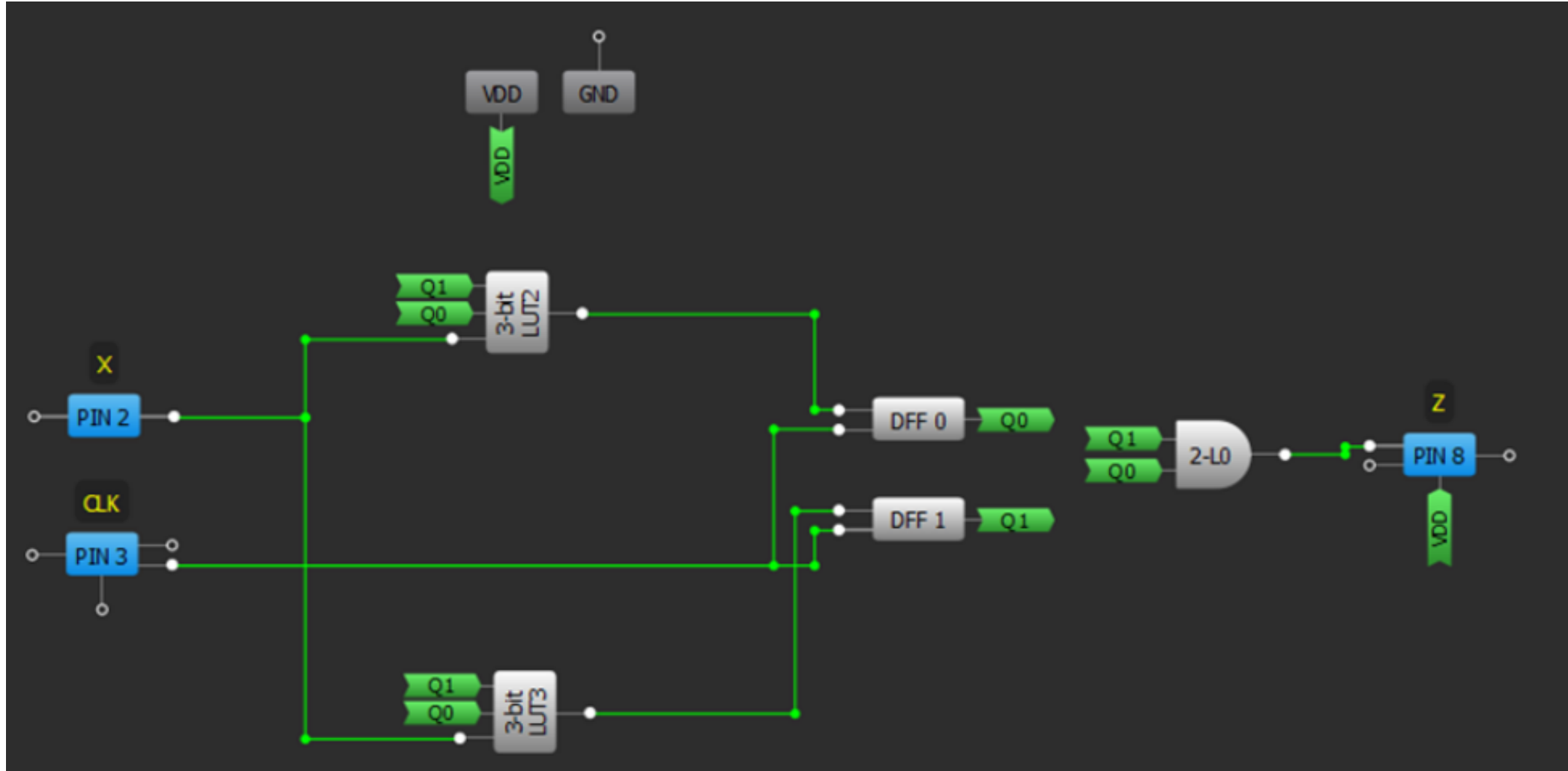

Case Study: Sequence Recognizer

Q1	Q0	X	D0
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

Table 2. D0 Truth Table

Q1	Q0	X	D1
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

Table 3. D1 Truth Table

Q1	Q0	Z
0	0	0
0	1	0
1	0	0
1	1	1

Table 4. Z Truth Table

Conclusion

- Simulation of simple circuits might be preferred over formal verification
- Formal verification
 - Highly time consuming
 - Error prone
 - Can provide guarantees for correctness
- LEAN3 is a useful proof assistance but not perfect
 - No easy forward recursion (termination must be guaranteed)
 - High memory usage
 - Handling arrays in proofs too complex
 - Limitations in automation
 - Great library of existing tactics

Challenges and Future Work

- Challenges
 - Learning how to use LEAN3 in a short time (steep learning curve)
 - Translating specifications into implementations
- Future Work:
 - Proof optimization (lower memory footprint)
 - Improving Automation
 - Specific library for Circuit Verification

Questions?



Universiteit
Leiden
The Netherlands